

17th Day

Posedge Detector

Design

```
module posedge_detect(input clk,a,output reg q, output y);
```

```
    wire y;
```

```
    always @(posedge clk)
```

```
    begin
```

```
        q<=a;
```

```
    end
```

```
    assign y=a & ~q;
```

```
endmodule
```

Testbench

```
module posedge_detect_tb();
```

```
    reg clk,a;
```

```
    wire q;
```

```
    wire y;
```

```
    posedge_detect dut(clk,a,q,y);
```


```
    always #5 clk=~clk;
```

```

initial
begin
  clk=0;
  a=0;
  #10;
  a=1;
  #10;
  a=0;
  #10;
  a=1;
end
endmodule

```

Simulation

 

Negedge Detector

Design

```
module negedge_detect(input clk,a,output reg q, output y);
```

```
    wire y;
```

```
    always @(posedge clk)
```

```
    begin
```

```
        q<=a;
```

```
    end
```

```
    assign y=~a & q;
```

```
endmodule
```

Testbench

```
module negedge_detect_tb();
```

```
    reg clk,a;
```

```
    wire q;
```

```
    wire y;
```

```
    negedge_detect dut(clk,a,q,y);
```

```
    always #5 clk=~clk;
```

```

initial
begin
clk=0;
a=0;
#10;
a=1;
#10;
a=0;
#10;
a=1;
#10;
a=0;
#50;
$finish;
end
endmodule

```

Simulation

