20th Day

Prime Detector Design

```
module prime(input [3:0]a,output reg prime);

always @(*)

begin

case(a)

4'd2,4'd3,4'd5,4'd7,4'd11,4'd13: prime=1'b1;

default:begin

prime=1'b0;

end

endcase
end
```

Testbench

endmodule

```
module prime_tb();

reg [3:0]a;

wire prime;

prime dut(a,prime);

initial

begin

repeat(20)
```

```
begin
a=$random;
#1;
if(prime==1'b1)
$display("at time=%0t, %d is prime",$time,a);
else
$display("at time=%0t, %d is not prime",$time, a);
end
end
```

endmodule

Simulation

```
at time=1,
              4 is not prime
at time=2,
              1 is not prime
at time=3,
              9 is not prime
              3 is prime
at time=4,
at time=5,
             13 is prime
at time=6,
             13 is prime
at time=7, at time=8,
              5 is prime
2 is prime
at time=9,
              1 is not prime
              13 is prime
at time=10,
at time=11,
               6 is not prime
at time=12,
              13 is prime
at time=13,
              13 is prime
              12 is not prime
9 is not prime
at time=14,
at time=15,
               6 is not prime
at time=16,
               5 is prime
at time=17,
at time=18,
              10 is not prime 5 is prime
at time=19,
at time=20,
               7 is prime
         Simulation
V C S
                                  Report
Time: 20 ns
                0.390 seconds;
                                       Data structure size:
                                                                0.0Mb
CPU Time:
```